

floydCycle_hardware

Proteus Simulation and Implementation of Floyd's cycle finding algorithm in a blockchain

Jishnu Das

Hobby project

IIT-BHU

29 June 2023

Outline

1. Theory
2. Cyclic Right Shifting
3. Problem Statement
4. Implementation Algorithm
5. Back of napkin sketch
6. Block Diagram
7. Sub-blocks
8. Entire Circuit Diagram
9. Links for Video Demonstration

Theory

- **What** is Blockchain - **Decentralized** (access to all) database of all transactions/ data.
- **How** is data stored
 - **Linked list** fashion. Generally the data is encrypted to ensure that no one can access it without authorization.
 - The list contains 2 elements - **data** and next data's **address**
- In our case, data is converted into binary and encrypted in a right cyclic shifting of the next node address by 3 bits

Cyclic Right Shifting

Unhashed Array:

[8,3,20,4,10,9,78,85,23,5,12,11,15,17,31,25,65,30,22,19,44,66,35,9]

4 = 0000100 -> hash -> 10000000 = 128

9 = 00001001 -> hash -> 00100001 = 33

12 = 00001100 -> hash -> 10000001 = 129 and similarly for the rest....

Corresponding Hashed array in the ROM:

[8,3,20,128,10,33,78,85,23,5,129,11,15,34,31,25,65,30,194,19,44,66,35,33]

Problem Statement


- **Data** will be in **unhashed 8 bits**. The **address** to the next data is **hashed 5 bits**
- We given this hashed array in the ROM.
- Probably someone has tampered with the data and there is a **cycle** in the linked list, which would collapse the entire linked list.
- Find if there is **any such cycle formed** and if present, find the decrypted **address of the head**.

Implementation Algorithm


■ Floyd Cycle Detection Algorithm

- Initialize 2 pointer - Fast and Slow pointer
- Move the fast pointer by two steps while slow pointer by 1 step

Initially both cars are at Node 1

 

 'Car M' is at Node 2
'Car B' is at Node 3



Implementation Algorithm


■ Algorithm

- ❑ **Initialize** them (fast ptr and slow ptr) to head of the linked list
- ❑ In the implementation the **fast pointer** goes by **one step in every clock cycle** and the **slow pointer** goes **one step in every two clock cycles**.




- ❑ Either fast pointer meets the end. The end pointer's address is 255 or 256. In this case **no loop is detected**.
- ❑ If **fast** pointer's **address** is **less** than **slow** pointer's **address**, then cycle is detected.
- ❑ The **address of the fast pointer** will determine the **address of head**.


Back of napkin block diagram

 


Block diagram

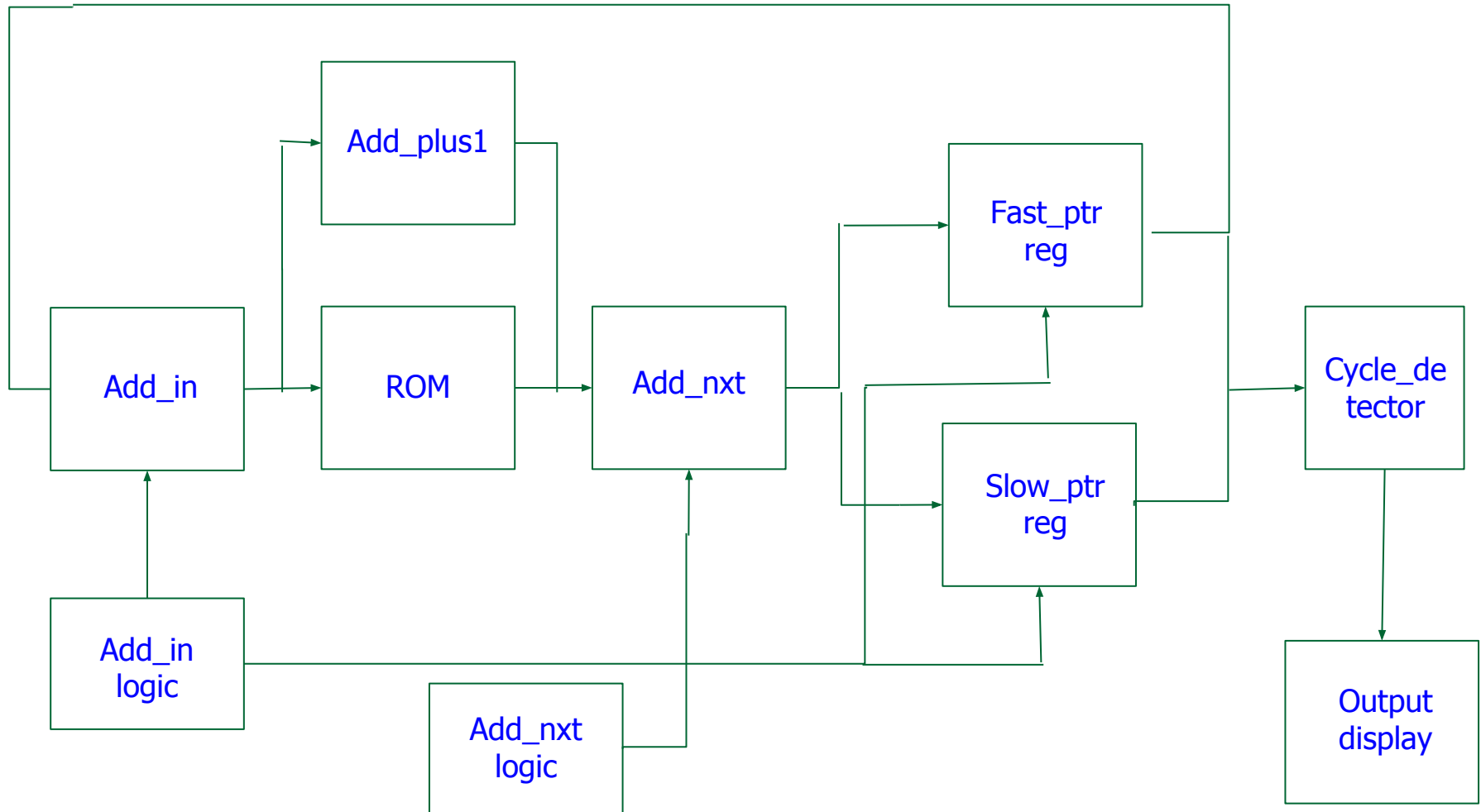


ROM block

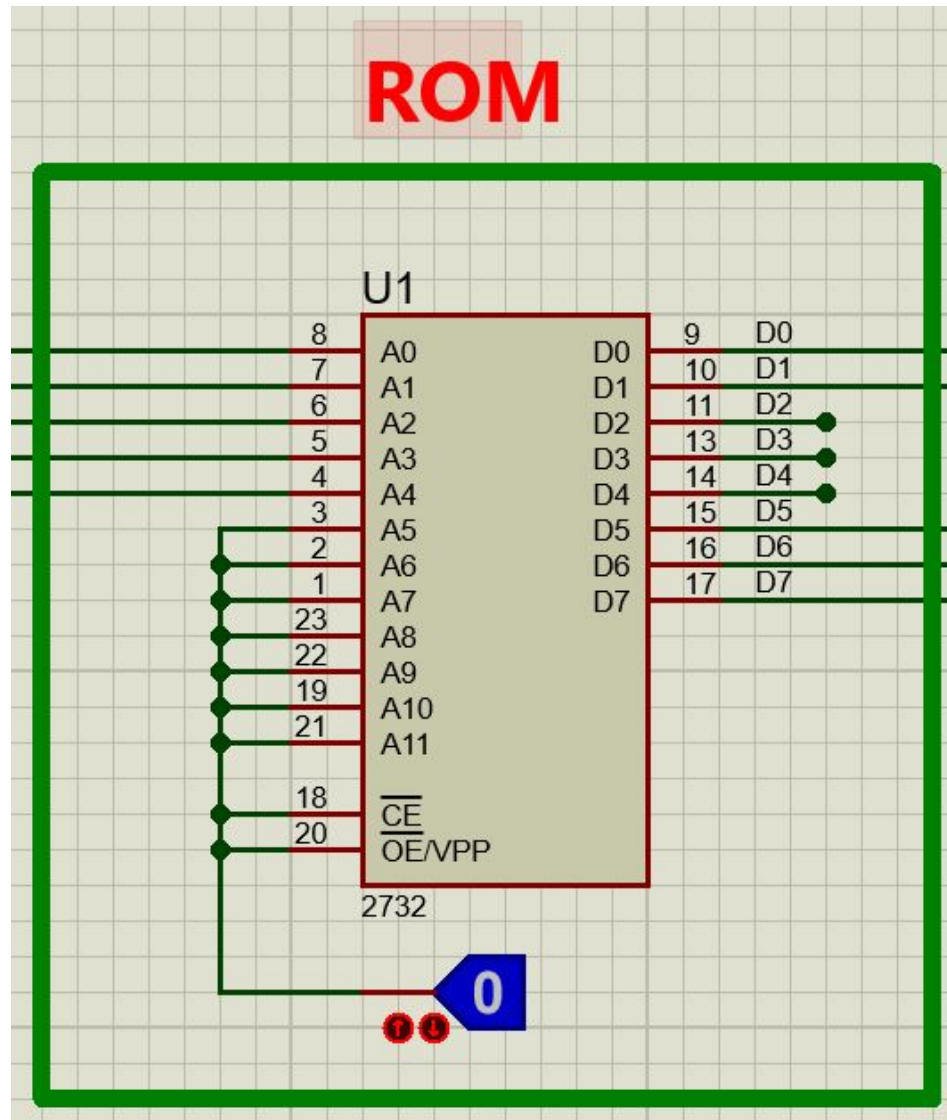


Add_nxt block

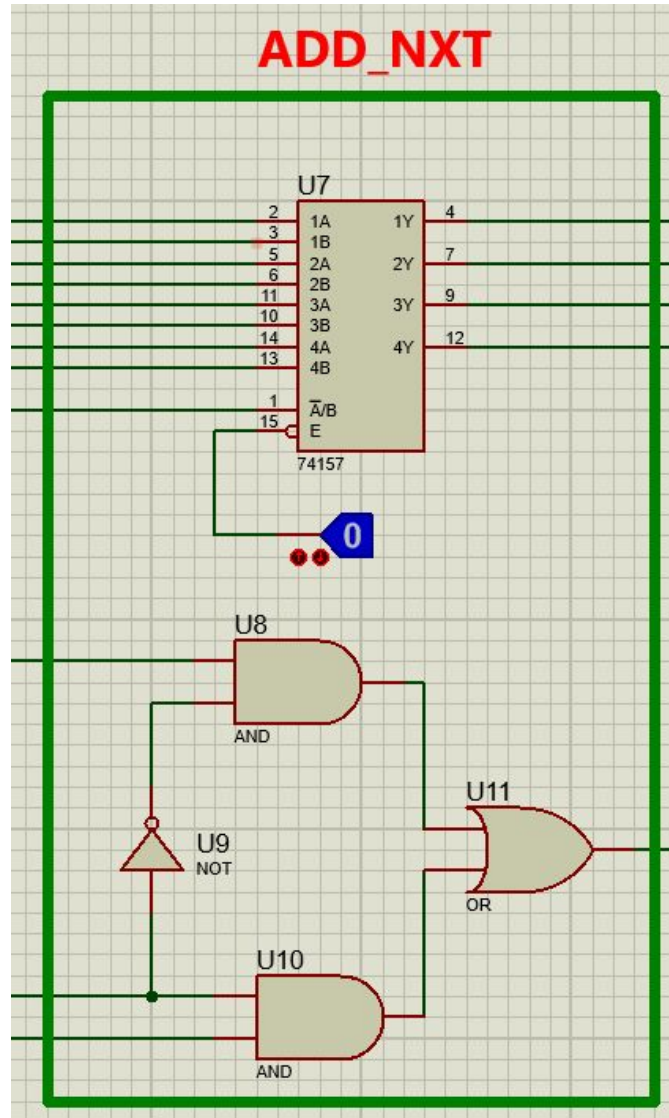


Add_plus1 block

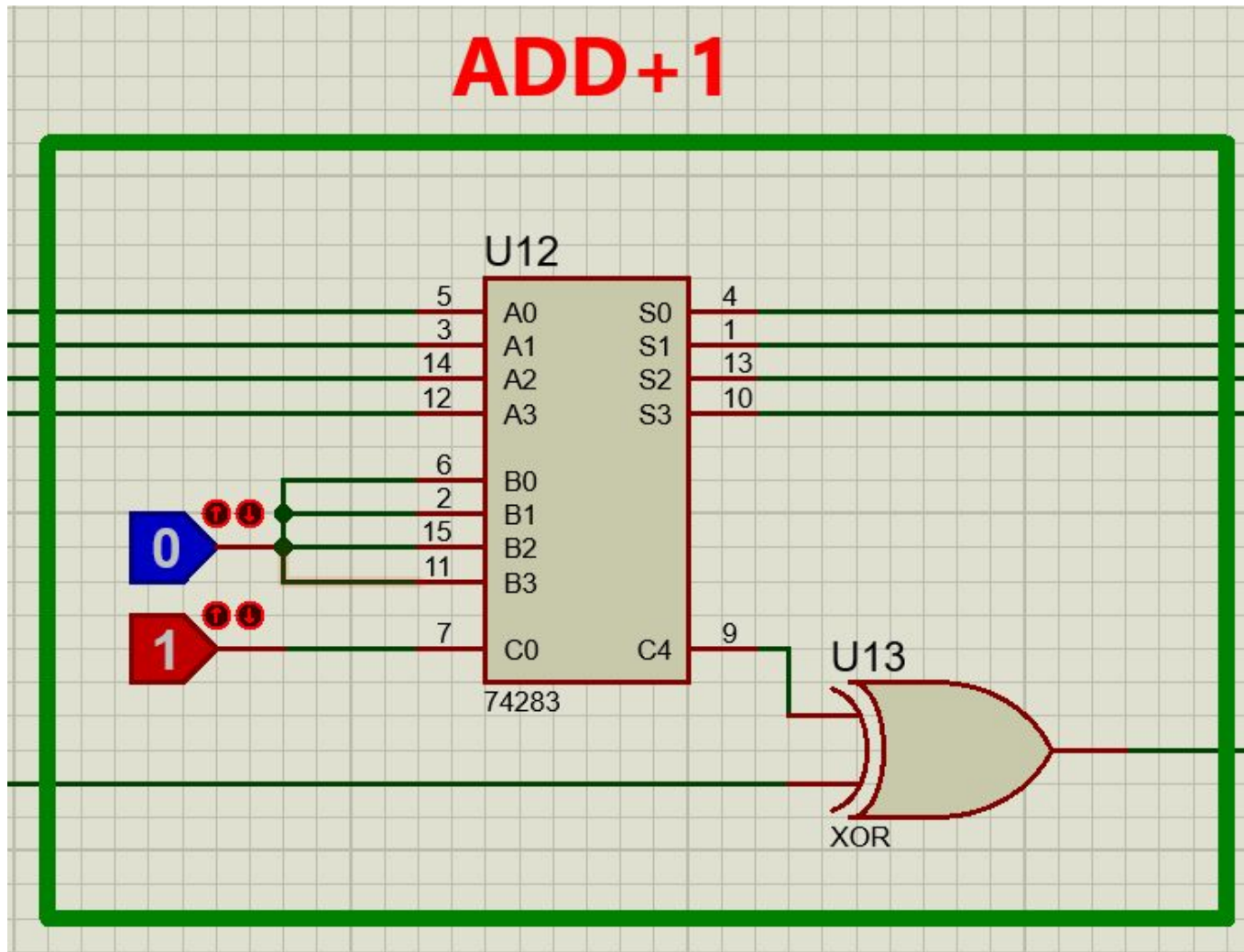


Add_nxt logic

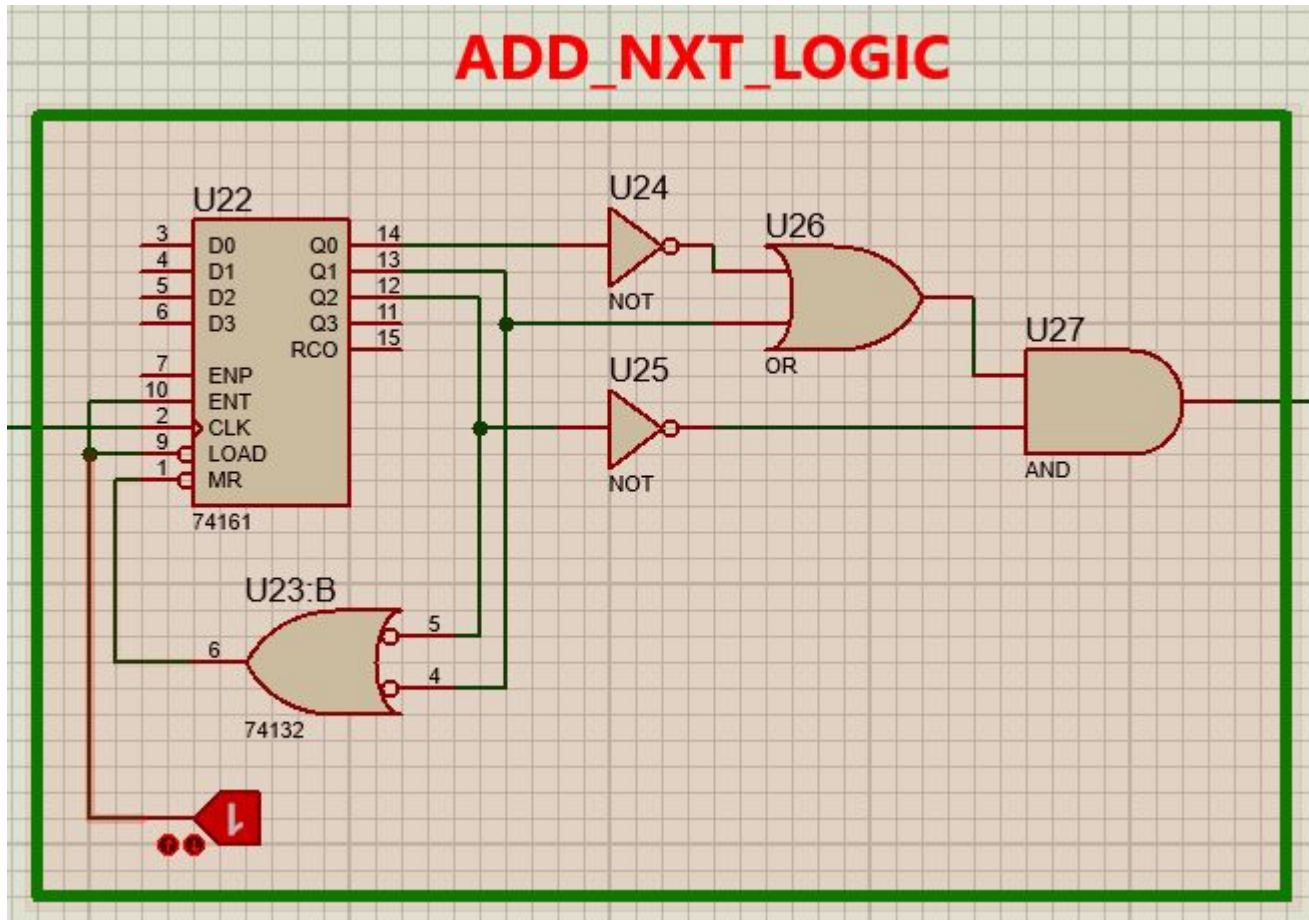


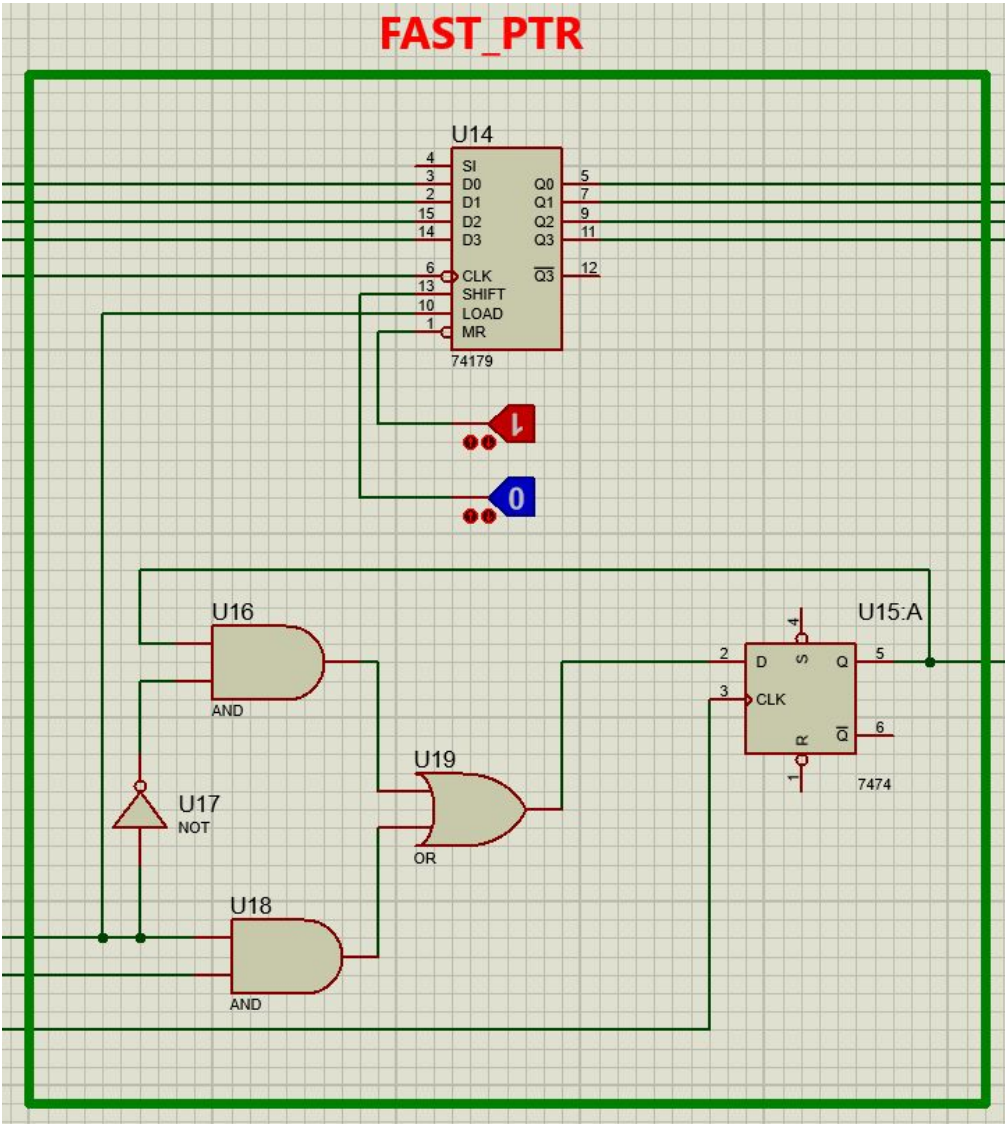


Slow_ptr reg

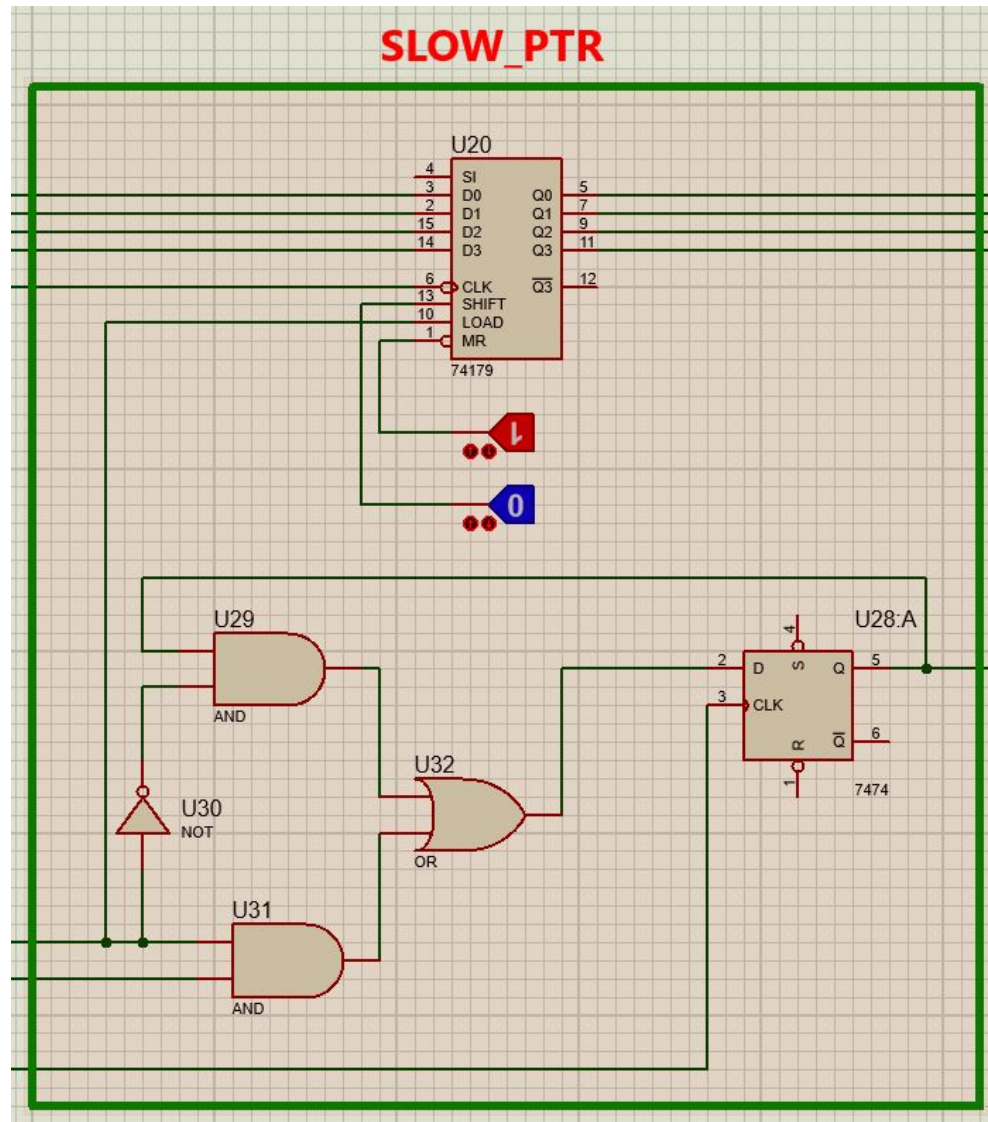

Cycle_detector logic

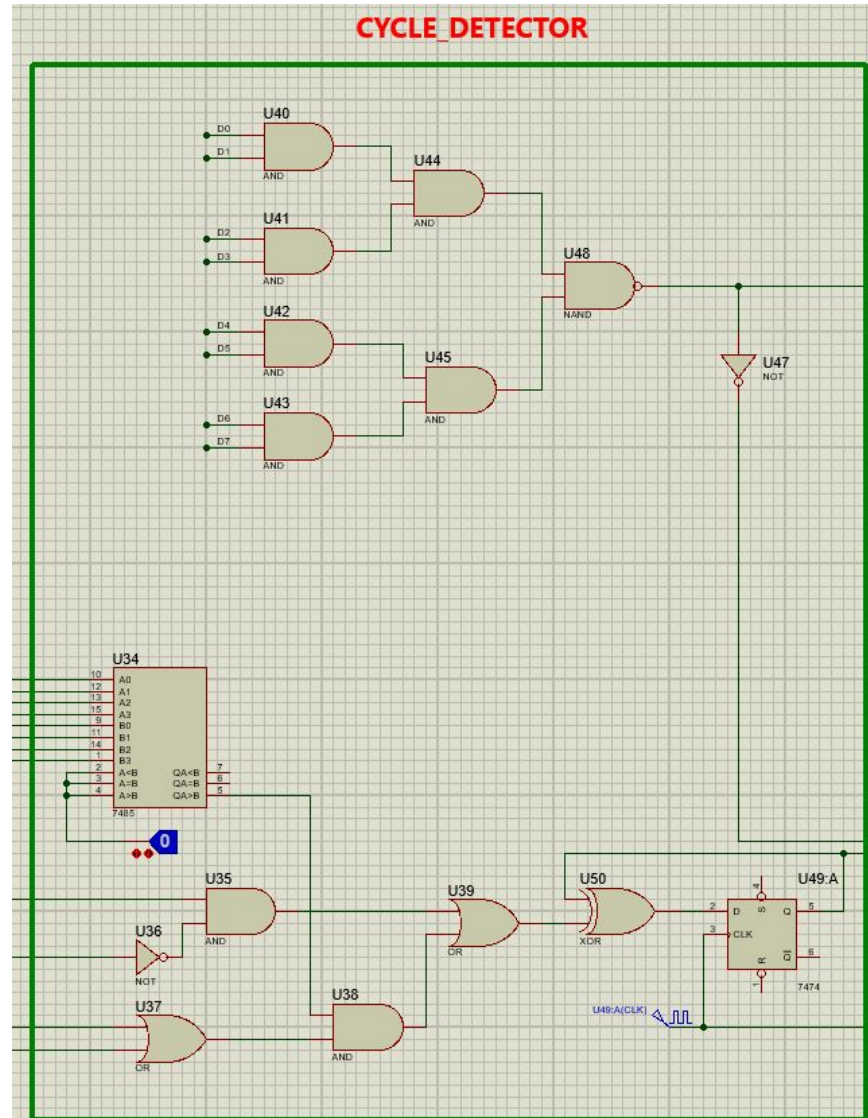

Entire Circuit Diagram

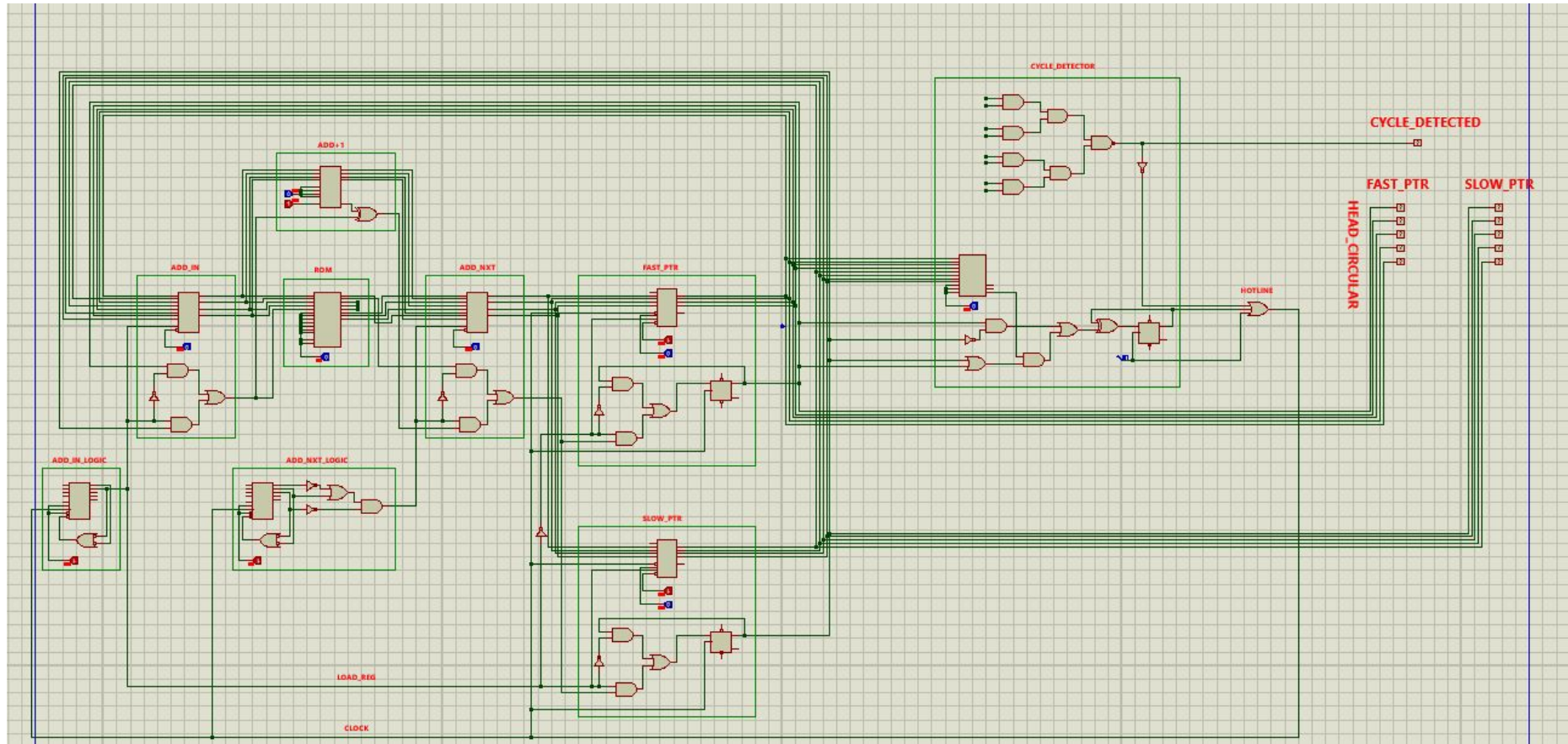

Links for Video Demonstration
